

Reconfigurable Systems



Jorge Semião

Instituto Superior de Engenharia

www.ualg.pt

Introduction HDL (Hardware Descrip. Language)

- Hardware description languages (HDL)
 - Language to describe hardware
 - Two popular languages
 - VHDL: **V**ery High Speed Integrated Circuits **H**ardware **D**escription **L**anguage
 - Developed by DOD (US Department Of Defence) from 1983
 - IEEE Standard 1076-1987/1993/200x
 - Based on the ADA language
 - Verilog
 - IEEE Standard 1364-1995/2001/2005
 - Based on the C language

Applications of HDL

- Model and document digital systems
 - Different levels of abstraction
 - Behavioral, structural, etc.
- Verify design
- Synthesize circuits
 - Convert from higher abstraction levels to lower abstraction levels


Introduction to VHDL

- VHSIC Hardware Description Language
 - VHSIC Very High Speed Integrated Circuit
 - Industrial Standard (IEEE-1076)
 - portability of designs
 - hierarchy in design description
 - technology independence

VHDL as a language


- strongly typed
 - type check at compile time
 - allows user defined types
 - case insensitive
 - two consecutive dashes (--) is used for comment

Level of Abstraction in VHDL

 

```
if Sel == 0
    Y <= A;
else
    Y <= B;
```

The block diagram of mux

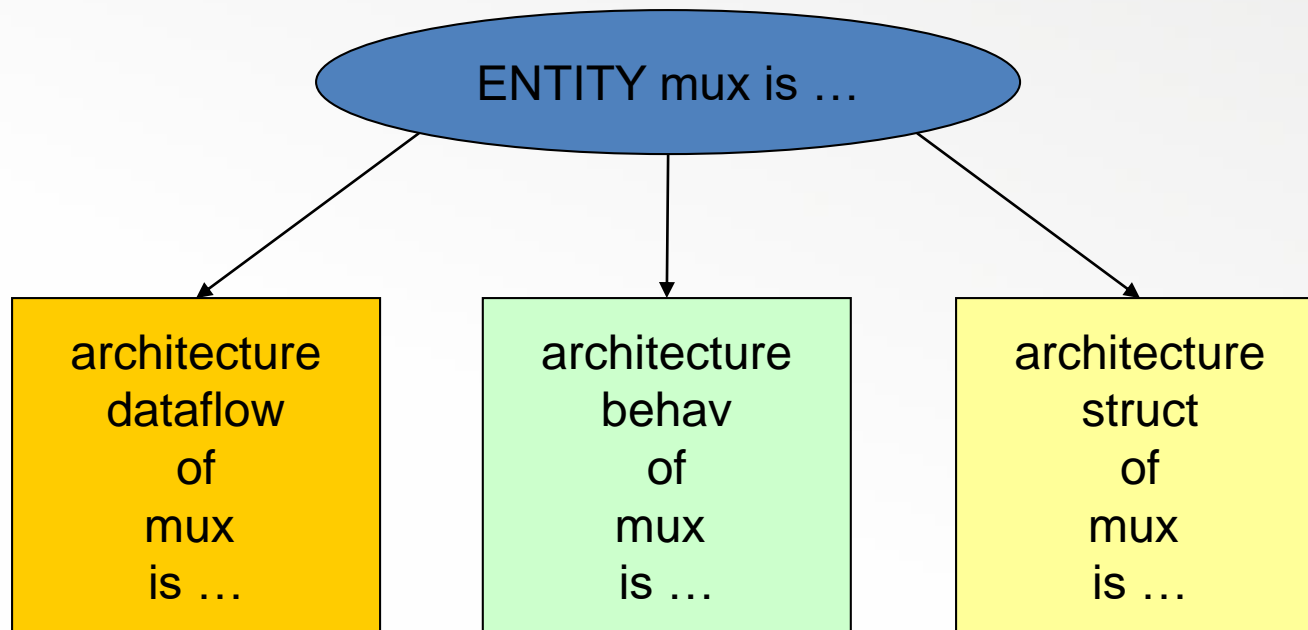

Entity

```
Entity mux is
  PORT (a, b, sel: in bit;
        y: out bit);
END mux;

ARCHITECTURE dataflow of mux IS
BEGIN
  y <= (sel and a) OR (NOT sel AND b);
END dataflow;
```

variable

mode

type

set of concurrent assignments to represent dataflow

Architecture Body

- Four modeling styles
 - concurrent assignments (dataflow)
 - interconnected component (structure)
 - sequential assignment statements (behavior)
 - combination of the above three

```
Example:  
ARCHITECTURE dataflow OF mux IS  
  
-- signals, variables declaration  
  
BEGIN  
...  
END dataflow;
```


Signals vs Variables

- Signals
 - Signals follow the notion of ‘event scheduling’
 - An event is characterized by a (time,value) pair
 - Signal assignment example:
 $X \leq X_{tmp};$ means
Schedule the assignment of the value of signal X_{tmp} to signal X
at (Current time + delta)
where delta: infinitesimal time unit used by simulator for
processing the signals

Signals vs Variables

- Variables
 - Variables do not have notion of 'events'
 - Variables can be defined and used only inside the **process** block and some other special blocks.
 - Variable declaration and assignment example:

```
process (...)  
variable K : bit;  
  begin  
    ...  
    -- Assign the value of sign  
immediately  
    K := L;  
    ...  
end process;
```

Variables can only be defined and used inside the **process** construct and can be defined only in this place

Dataflow

- concurrent signal assignment statements include:
 - simple signal assignment (\leq)
 - select signal statement
 - conditional signal statement

Dataflow

- simple signal assignment
 $y \leftarrow (\text{sel AND } a) \text{ OR } (\text{NOT sel AND } b);$
 - y : target signal
 - \leftarrow : signal assignment operator
 - six logical operators are
 - AND OR NAND NOR XOR NOT
 - relational operators
 - $=, \neq, <, \leq, >, \geq$

Dataflow

- Selected Signal Assignment
 - concurrent signal

```
ENTITY mux_df IS
    PORT (a, b, sel: in bit;
          y: out bit);
END mux_df;

ARCHITECTURE dataflow of mux_df IS
BEGIN
    WITH sel SELECT
        y <= a when '1',
            b when '0';
END dataflow;
```

Dataflow

```
Entity mux2_df is
    PORT ( data : in BIT_VECTOR(3 DOWNT0 0);
           sel: in INTEGER RANGE 0 to 3;
           f: out bit);
END mux2_df;

ARCHITECTURE dataflow of mux2_df IS
BEGIN
    WITH sel SELECT
        f <= data(0) when 0,
           data(1) when 1,
           data(2) when 2,
           data(3) when 3;
END dataflow;
```

BIT_VECTOR is an array of bits which is of type BIT

Dataflow

```
library ieee;
use ieee.std_logic_1164.all;


entity dcd_3_8 is
    port (
        a: in std_logic_vector(2 downto 0);
        s: out std_logic_vector(7 downto 0)
    );
end dcd_3_8;

architecture dataflow of dcd_3_8 is
begin
    with a SELECT
        s <= "00000001" when "000",
            "00000010" when "001" | "00Z",
            "00000100" when "010" | "0Z0",
            "00001000" when "011" | "0ZZ",
            "00010000" when "100" | "Z00",
            "00100000" when "101" | "Z0Z",
            "01000000" when "110" | "ZZ0",
            "10000000" when "111" | "ZZZ",
            "xxxxxxxx" when OTHERS;
end dataflow;
```

Dataflow

```

 
type STD_LOGIC is (
    'U' – uninitialized
    'X' – Forcing unknown
    '0' – Forcing low
    '1' – Forcing high
    'Z' – High Impedance
    'W' – Weak Unknown
    'L' – Weak Low
    'H' – Weak High
    '-' – Don't Care
);
  
```



Tri-state Buffer

Din	OE	Dout
X	0	Z
0	1	0
1	1	1

Dataflow

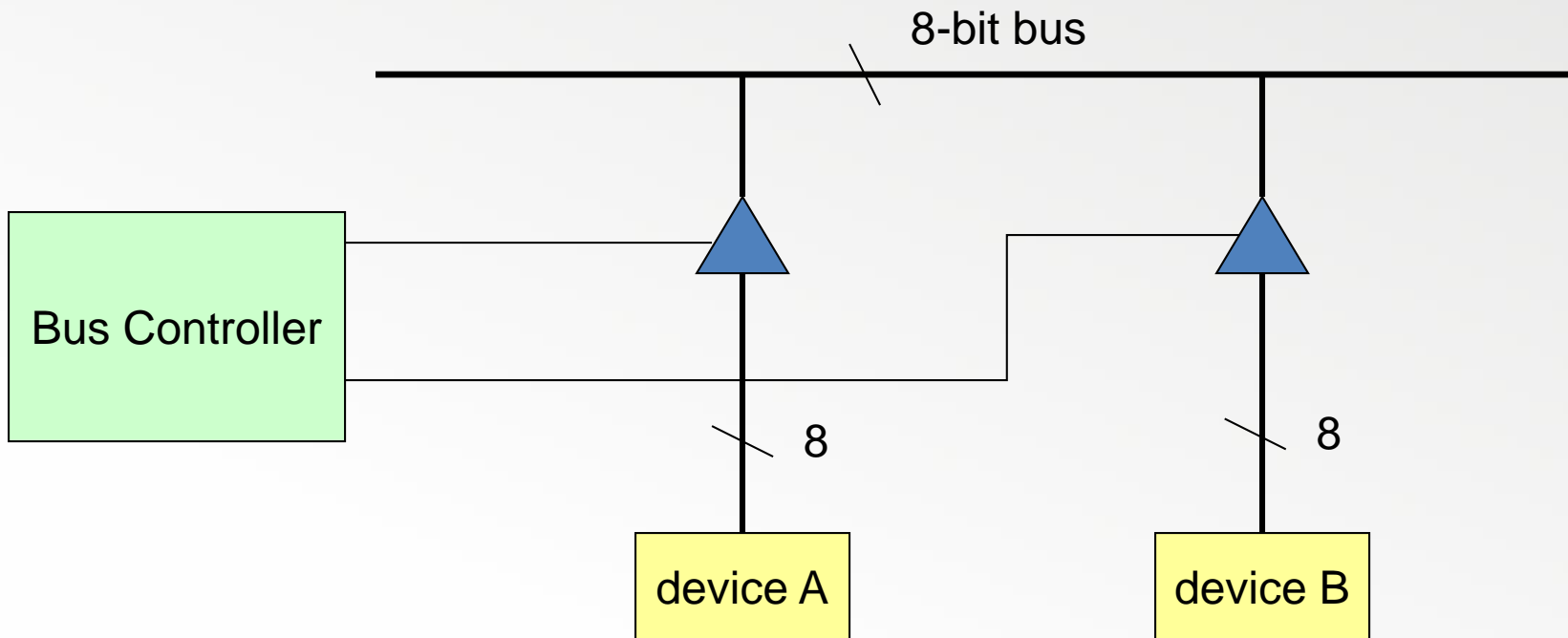

Dataflow

Conditional Signal Assignment

```
ENTITY mux_df2 IS
    port ( a, b, sel : in bit;
          y : out bit );
END mux_df2;

ARCHITECTURE dataflow of mux_df2 is
BEGIN
    y <= a WHEN sel = '1' ELSE b;
END dataflow;
```

Dataflow


```
Entity mux2_df is
    PORT ( data : in BIT_VECTOR(3 DOWNT0 0);
           sel: in INTEGER RANGE 0 to 3;
           f: out bit);
END mux2_df;

ARCHITECTURE dataflow of mux2_df IS
BEGIN
    f <= data(0) when sel = 0 ELSE,
        data(1) when sel = 1 ELSE,
        data(2) when sel = 2 ELSE,
        data(3);
END dataflow;
```

When a conditional signal assignment statement is simulated, each Boolean expression is tested in the order that it was written.

Dataflow

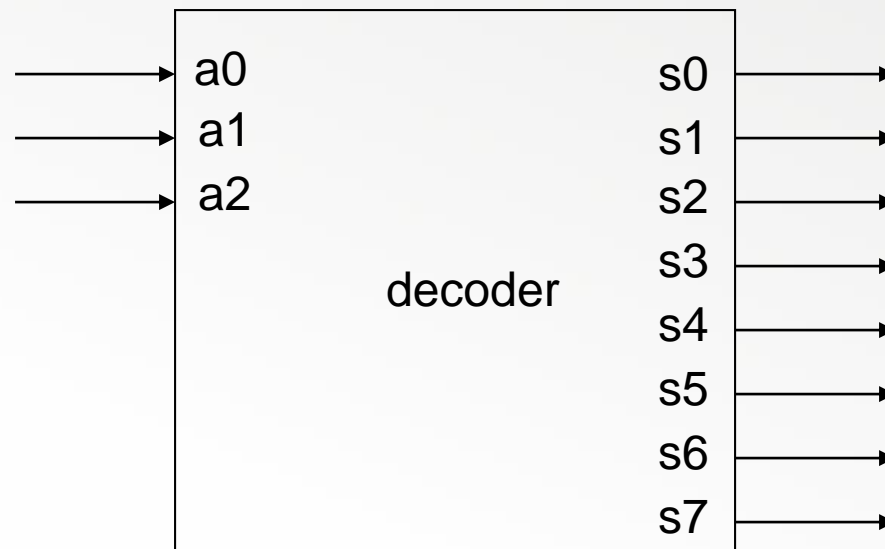- Decoder is another example of selected signal assignment construct



Behavioral Descriptions

- contain “PROCESS” statement.
 - statements appearing inside a process are simulated sequentially. However, a process statement is a concurrent statement.
 - also contain a sensitivity list or WAIT statement.
 - variables can be used locally (keyword VARIABLE).
 - := is used for a variable assignment.
- can contain multiple processes.
 - signals are used for communication
 - information can only be transferred between processes through signals.

Behavioral

```
ENTITY mux_proc IS port (a, b, sel: in bit;  
                        y: out bit);  
END mux_proc;  
architecture behv of mux_proc is  
begin  
  PROCESS (a, b, sel)  
  BEGIN  
    IF(sel = '0') THEN  
      y <= b;  
    ELSIF(sel = '1') THEN  
      y <= a;  
    END IF;  
  END PROCESS;  
END behv;
```

Behavioral


```
ENTITY unknown IS port (a, b: in bit;  
                        y, z: out bit);  
END unknown;  
architecture behv of unknown is  
begin  
  PROCESS (a, b)  
  BEGIN  
    IF((a or b) = '0') THEN  
      y <= '1';  
    ELSE  
      z <= a or b;  
    END IF;  
  END PROCESS;  
END behv;
```

Look at differences
between simulation and
synthesis.

Behavioral

```

ENTITY dff_mux2 IS
    port (reset, clock, din, sel: in std_logic;
          dout : out std_logic);
END dff_mux2;
architecture inference of dff_mux2 is
    signal q_out1, q_out2: std_logic;
begin
    PROCESS -- no sensitivity list here
    BEGIN
        WAIT_UNTIL (clock'EVENT and clock = '1');
        q_out1 <= din;
        q_out2 <= q_out1;
    END PROCESS;
    dout <= q_out1 when sel = '1' else q_out2;
END inference;
  
```

 

Built-in Datatypes

- Scalar (single valued) signal types:
 - `bit`
 - `boolean`
 - `integer`
 - Examples:
 - `A: in bit;`
 - `G: out boolean;`
 - `K: out integer range -2**4 to 2**4-1;`
- Aggregate (collection) signal types:
 - `bit_vector`: array of bits representing binary numbers
 - `signed`: array of bits representing signed binary numbers
 - Examples:
 - `D: in bit_vector(0 to 7);`
 - `E: in bit_vector(7 downto 0);`
 - `M: in signed (4 downto 0);`
 `--signed 5 bit_vector binary number`

User-defined datatype

- Construct datatypes arbitrarily or using built-in datatypes
- Examples:
 - `type temperature is (high, medium, low);`
 - `type byte is array(0 to 7) of bit;`

VHDL Architecture

- VHDL description (sequential behavior):

```
architecture arch_name of my_ckt is
begin
  p1: process (A,B,S)
  • begin
    if (S='0') then
      X <= A;
    else
      X <= B;
    end if;

    if ((X = '0') and (S = '0')) then
      Y <= '1';
    else
      Y <= '0';
    end if;

    end process p1;
end;
```



Error: Signals defined as output ports can only be driven and not read

VHDL Architecture

architecture behav_seq of my_ckt is

```

signal Xtmp: bit;

begin
  p1: process (A,B,S,Xtmp)
  begin
    if (S='0') then
      Xtmp <= A;
    else
      Xtmp <= B;
    end if;

    if ((Xtmp = '0') and (S = '0')) then
      Y <= '1';
    else
      Y <= '0';
    end if;

    X <= Xtmp;
  end process p1;
end;
```

Signals can only be defined in this place before the **begin** keyword

General rule: Include all signals in the sensitivity list of the process which either appear in relational comparisons or on the right side of the assignment operator inside the process construct.

In our example:

Xtmp and **S** occur in relational comparisons

A, **B** and **Xtmp** occur on the right side of the assignment operators

VHDL Architecture

- VHDL description (concurrent behavior):

```
architecture behav_conc of my_ckt is
```

```
    signal Xtmp: bit;
```

```
begin
```

```
    Xtmp <= A when (S='0') else  
            B;
```

```
    Y <= '1' when ((Xtmp = '0') and (S = '0')) else  
            '0';
```

```
    X <= Xtmp;
```

```
end ;
```

Structural level netlist

architecture behav_conc of my_ckt is

-- component declarations

signal Sbar, Xbar, W1, W2: bit;

begin

G1: not port map(Sbar,S) ;

G2: and port map(W1,A,Sbar) ;

G3: and port map(W2,B,S) ;

G4: or port map(X,W1,W2) ;

G5: not port map(Xbar,X) ;

G6: and port map(Y,Xbar,Sbar) ;

end ;

- Gate level VHDL descriptions (**and**, **or**, etc) are described separately
- Design in which other design descriptions are included is called a "hierarchical design"
- A VHDL design is included in current design using port map statement