

Reconfigurable Systems



Jorge Semião


Instituto Superior de Engenharia

www.ualg.pt


Assignment 2

- Implement in VHDL a sender and receiver stream cipher using 8-bit LFSR as key stream generator
- Implement one entity for the encryption and another for the decryption, to encrypt/decrypt 8 bits
- Simulate both entities together
- Create random words (8-bits) to be the transmitting data, and simulate the encryption, sending, decryption and data confirmation
- Use a single XOR gate as a cipher algorithm, to encrypt and decrypt data with the key stream

Stream Cipher diagram

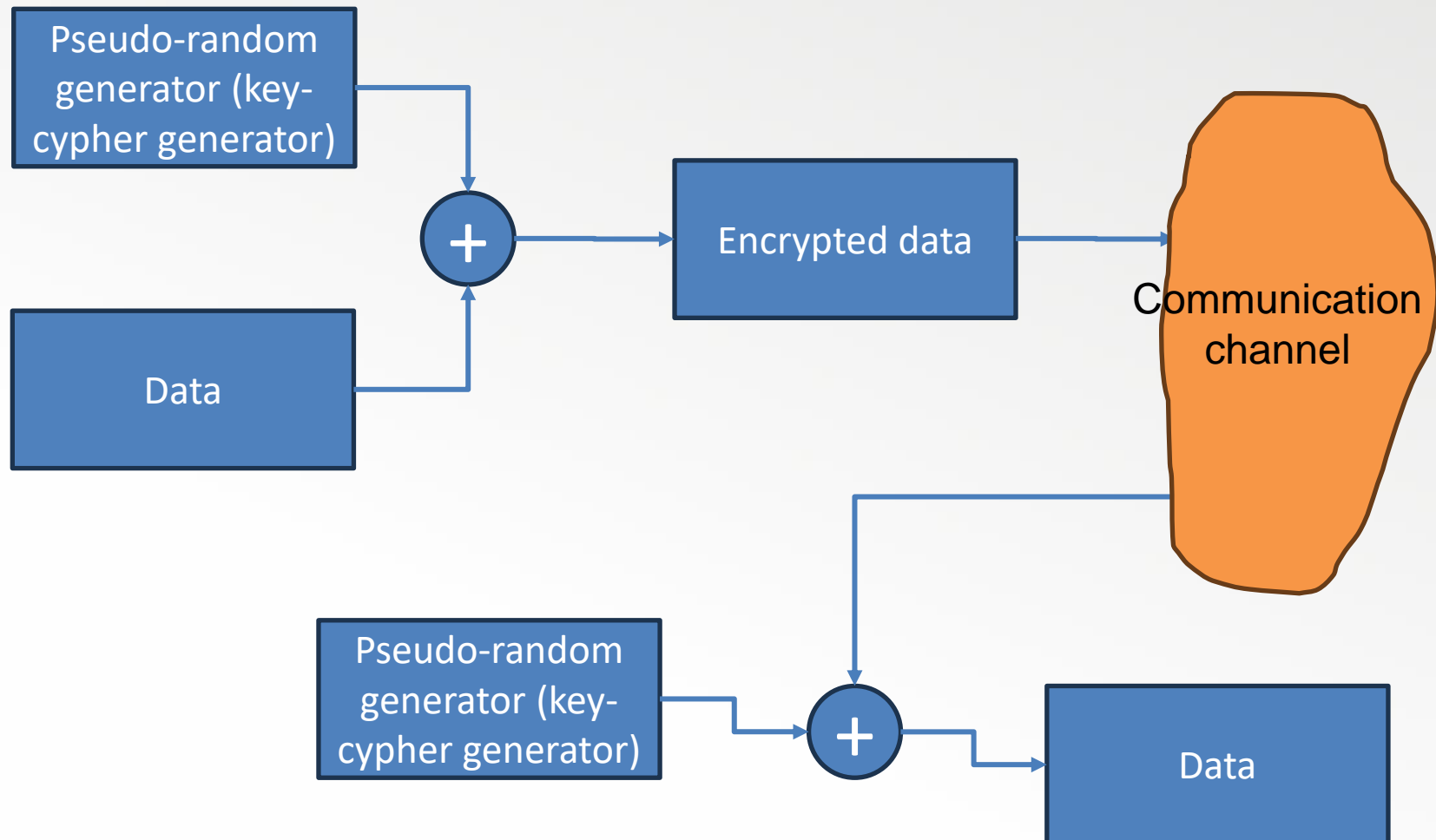


Stream Cipher diagram

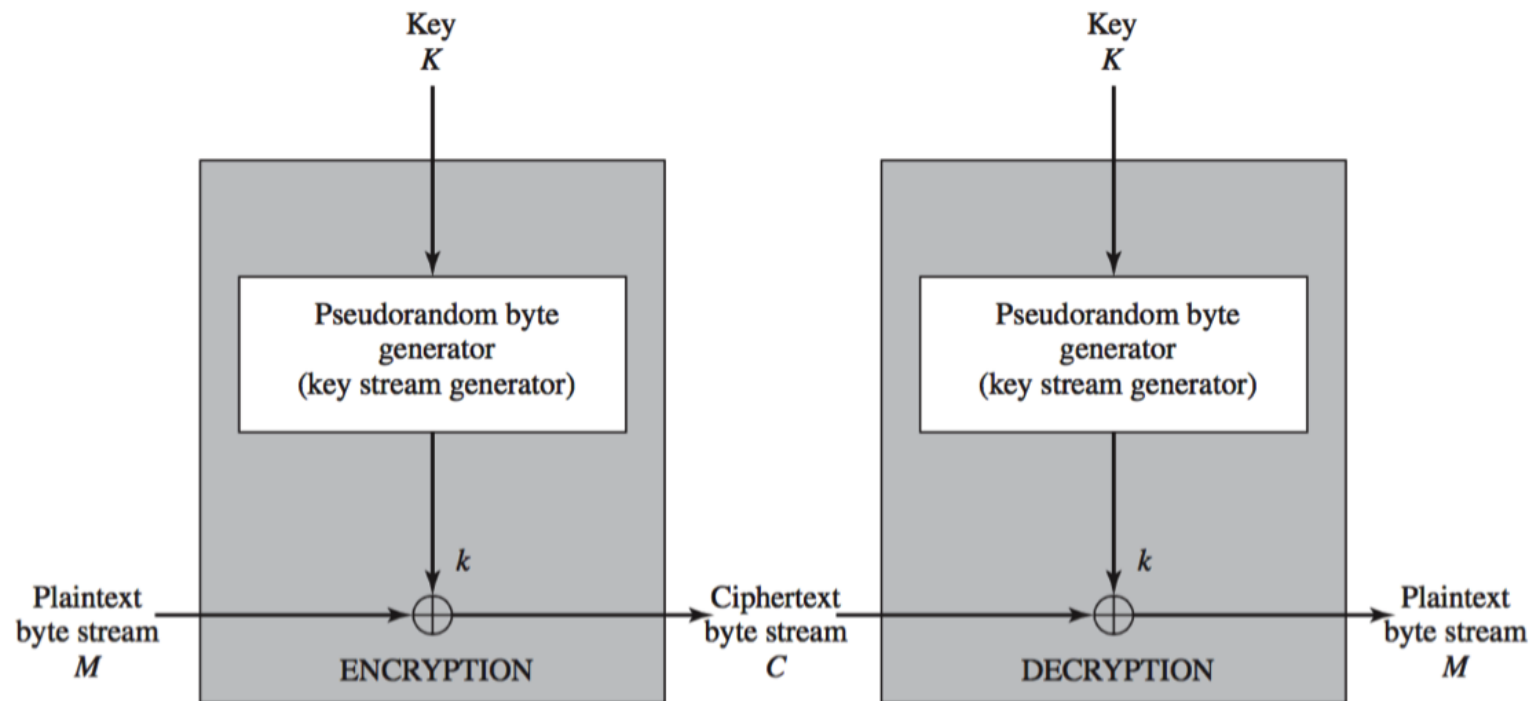


LFSR (Linear Feedback Shift-Register)

- Pseudo-random generator
- Only specific feedback loops generate $2^n - 1$ pseudo-random patterns (other loops are not used)
- May act as a key stream generator in cryptography
- A different seed will produce different patterns
- Two possible architectures: Linear or Modular


 
LFSR (Linear Feedback Shift-Register) – Linear type (or Fibonacci)



 
LFSR (Linear Feedback Shift-Register) – Modular type (or Galois)



LFSR examples

 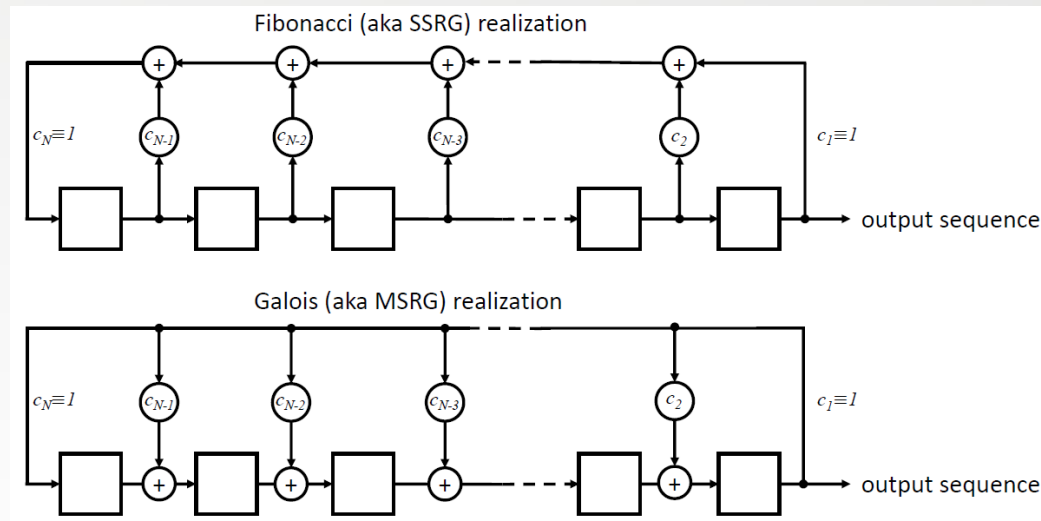

圖一：Fibonacci LFSR

 


圖二：Galois LFSR

LFSR – Primitive polynomial


- The feedback loops that generate $2^n - 1$ different patterns
- Ex: $x^4 + x^1 + 1^0$ is a 4-bit LFSR with loops in FF 1 and 0

1: 0	13: 4 3 1 0	25: 3 0
2: 1 0	14: 12 11 1 0	26: 8 7 1 0
3: 1 0	15: 1 0	27: 8 7 1 0
4: 1 0	16: 5 3 2 0	28: 3 0
5: 2 0	17: 3 0	29: 2 0
6: 1 0	18: 7 0	30: 16 15 1 0
7: 1 0	19: 6 5 1 0	31: 3 0
8: 6 5 1 0	20: 3 0	32: 28 27 1 0
9: 4 0	21: 2 0	33: 13 0
10: 3 0	22: 1 0	34: 15 14 1 0
11: 2 0	23: 5 0	35: 2 0
12: 7 4 3 0	24: 4 3 1 0	36: 11 0

LFSR – Primitive polynomial

 



Internal Feedback/Type I
LFSR

 

External Feedback/Type II
LFSR

$$P(x) = x^0 + x^1 + x^3 + x^4$$

LFSR – Primitive polynomial

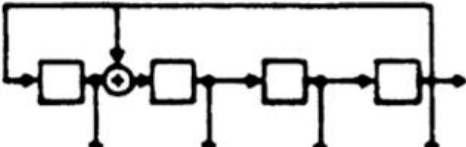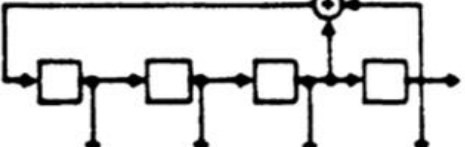IE Type						EE Type					
$X^4 + X + 1$						$X^4 + X + 1$					
											
Clock	A ⁰	A ¹	A ²	A ³	Decimal Value	A ⁰	A ¹	A ²	A ³	Decimal Value	
Initial State	0	0	0	1	—	0	0	0	1	—	
1	1	1	0	0	12	1	0	0	0	8	
2	0	1	1	0	6	0	1	0	0	4	
3	0	0	1	1	3	0	0	1	0	2	
4	1	1	0	1	13	1	0	0	1	9	
5	1	0	1	0	10	1	1	0	0	12	
6	0	1	0	1	5	0	1	1	0	6	
7	1	1	1	0	14	1	0	1	1	11	
8	0	1	1	1	7	0	1	0	1	5	
9	1	1	1	1	15	1	0	1	0	10	
10	1	0	1	1	11	1	1	0	1	13	
11	1	0	0	1	9	1	1	1	0	14	
12	1	0	0	0	8	1	1	1	1	15	
13	0	1	0	0	4	0	1	1	1	7	
14	0	0	1	0	2	0	0	1	1	3	
15	0	0	0	1	1	0	0	0	1	1	
16	1	1	0	0	12	1	0	0	0	8	